

Project 7: Carry Select Adders

A Comprehensive Study of Advanced Digital Circuits

By: Abhishek Sharma , Nikunj Agrawal , Ayush Jain , Gati Goyal

Created By Team Alpha

Contents

1	Introduction	3
2	Structure and Operation	3
3	Example: 16-bit Carry Select Adder	3
4	Synthesis Design	3
5	Circuit Diagram	3
6	RTL Code	4
6.1	Testbench	4
7	Simulation Results	5
8	Schematic	6
9	Advantages	6
10	Disadvantages	6
11	Applications	6
12	Conclusion	6

Created By Team Alpha

1 Introduction

A Carry Select Adder (CSA) is a high-speed adder used in digital circuits to improve the speed of binary addition. It achieves this by precomputing the sum and carry outputs for both possible values of the carry-in, allowing the correct result to be quickly selected once the actual carry-in is known.

2 Structure and Operation

The Carry Select Adder divides the addition process into several smaller sub-adders, each responsible for a portion of the total bit-width. Each sub-adder performs two parallel additions for each possible carry-in (0 and 1), and the final result is selected based on the actual carry-in.

1. **Division into Blocks:** The adder is divided into multiple blocks, each handling a portion of the bits.
2. **Dual Addition Paths:** Each block computes two possible sums and carries:
 - One assuming the carry-in is 0.
 - One assuming the carry-in is 1.
3. **Multiplexers for Selection:** Once the actual carry-in for a block is known, a multiplexer selects the correct sum and carry-out based on this carry-in.

3 Example: 16-bit Carry Select Adder

Consider a 16-bit Carry Select Adder divided into four blocks, each containing 4 bits.

1. **Block 1 (Bits 0-3):**
 - Computes the sum and carry for bits 0-3 assuming carry-in is 0.
 - Computes the sum and carry for bits 0-3 assuming carry-in is 1.
2. **Block 2 (Bits 4-7):**
 - Computes the sum and carry for bits 4-7 assuming carry-in is 0.
 - Computes the sum and carry for bits 4-7 assuming carry-in is 1.
3. **Block 3 (Bits 8-11):**
 - Computes the sum and carry for bits 8-11 assuming carry-in is 0.
 - Computes the sum and carry for bits 8-11 assuming carry-in is 1.
4. **Block 4 (Bits 12-15):**
 - Computes the sum and carry for bits 12-15 assuming carry-in is 0.
 - Computes the sum and carry for bits 12-15 assuming carry-in is 1.

Each block has two outputs for sums and carries: one for carry-in 0 and one for carry-in 1. The actual carry-in for each block is determined by the carry-out of the previous block, selected using a multiplexer.

4 Synthesis Design

5 Circuit Diagram

The circuit diagram for a Carry Select Adder includes:

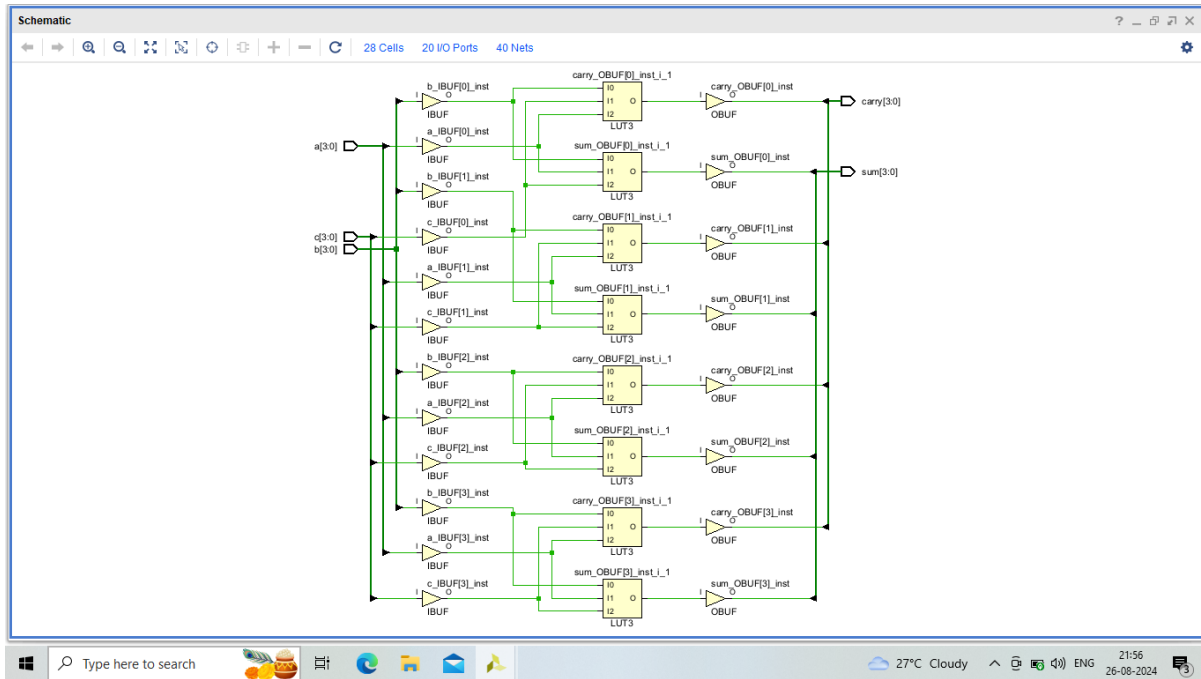


Figure 1: Synthesis of Carry Select Adder

Block 1:	Block 2:	Block 3:	Block 4:
RCA0	RCA0	RCA0	RCA0
RCA1	RCA1	RCA1	RCA1
Mux	Mux	Mux	Mux

6 RTL Code

Listing 1: Carry Save Adder RTL Code

```

1 module carry_save_adder #(parameter N = 4) (
2     input logic [N-1:0] a,
3     input logic [N-1:0] b,
4     input logic [N-1:0] c,
5     output logic [N-1:0] sum,
6     output logic [N-1:0] carry
7 );
8
9     assign sum = a ^ b ^ c;
10    assign carry = (a & b) (b & c) (c & a);
11
12 endmodule

```

6.1 Testbench

Listing 2: 32 bit Adder Testbench

```

1 module tb_carry_save_adder;
2
3     parameter N = 4;
4     logic [N-1:0] a, b, c;
5     logic [N-1:0] sum, carry;

```

```

6
7    carry_save_adder #(N) csa (.a(a), .b(b), .c(c), .sum(sum),
    .carry(carry));
8
9    initial begin
10       // Test cases
11       a = 4'b0011; b = 4'b0101; c = 4'b0110; #10;
12       $display("A = %b, B = %b, C = %b, SUM = %b, CARRY = %b", a, b,
           c, sum, carry);
13
14       a = 4'b1111; b = 4'b0001; c = 4'b0001; #10;
15       $display("A = %b, B = %b, C = %b, SUM = %b, CARRY = %b", a, b,
           c, sum, carry);
16
17       a = 4'b1001; b = 4'b1001; c = 4'b1001; #10;
18       $display("A = %b, B = %b, C = %b, SUM = %b, CARRY = %b", a, b,
           c, sum, carry);
19
20       $finish;
21    end
22
23 endmodule

```

7 Simulation Results

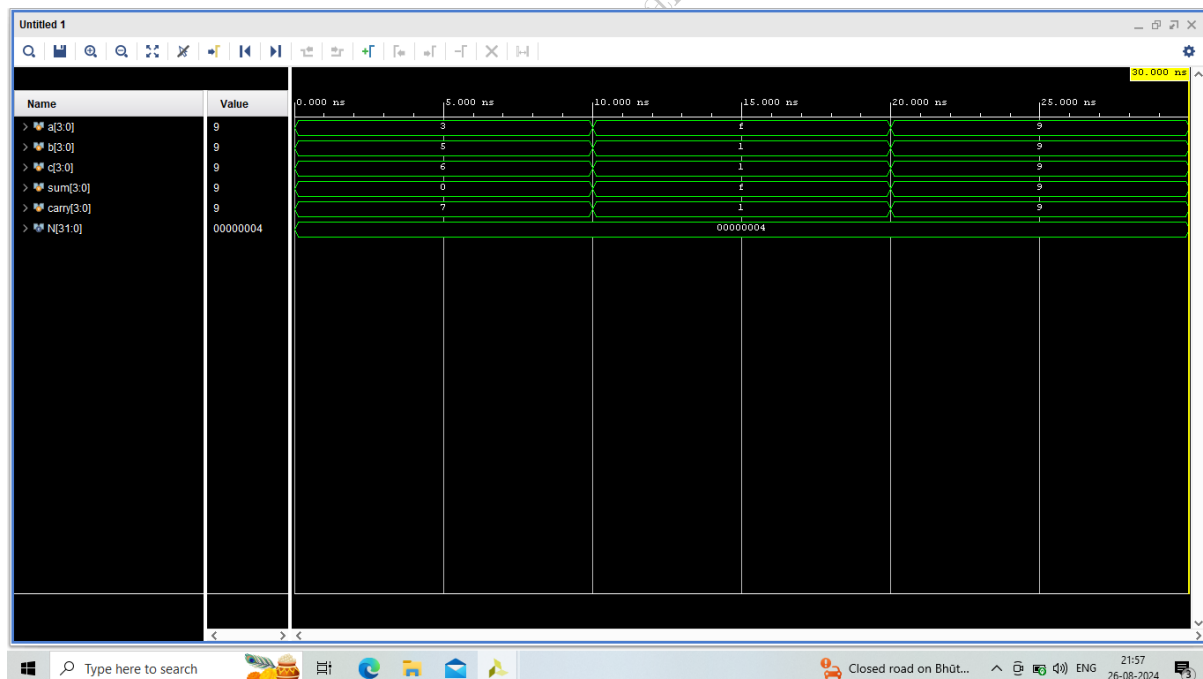


Figure 2: Simulation results of Carry Select Adder

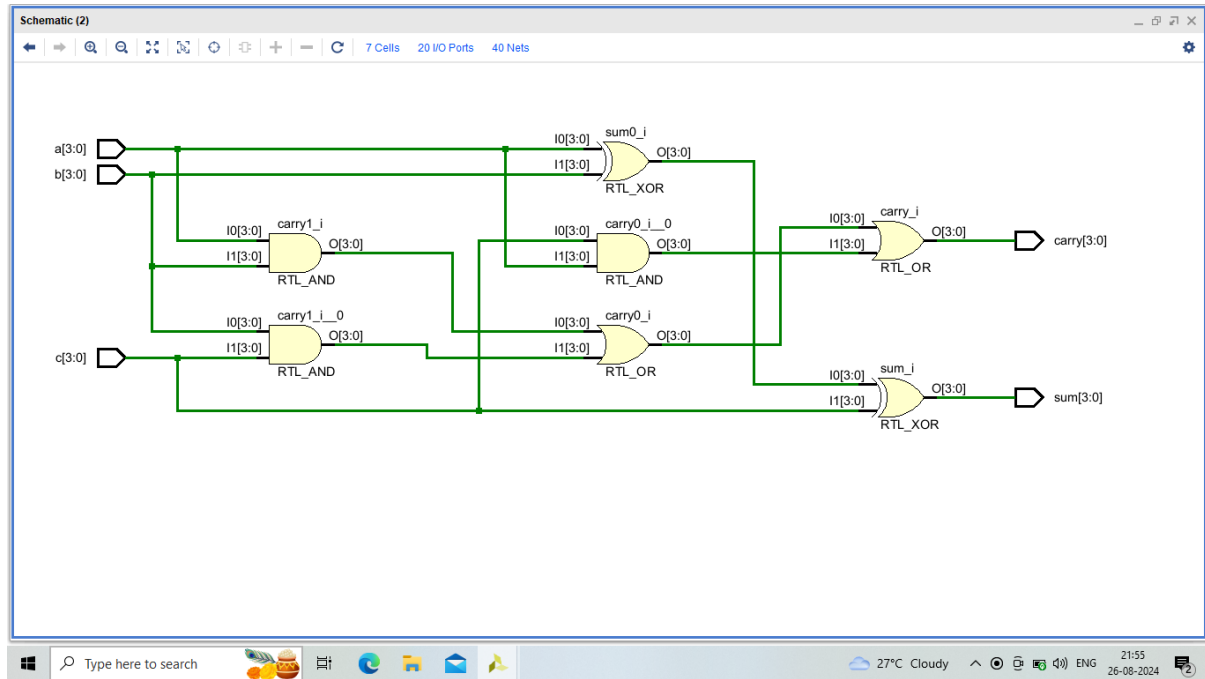


Figure 3: Schematic of Carry Select Adder

8 Schematic

9 Advantages

- **Speed:** By precomputing results for both possible carry-in values, the Carry Select Adder significantly reduces the critical path delay compared to a simple Ripple Carry Adder.
- **Scalability:** The design can be easily scaled to larger bit-widths by adding more blocks.

10 Disadvantages

- **Area and Power:** The duplication of hardware to compute results for both carry-in values increases the area and power consumption.

11 Applications

- **High-Speed Arithmetic Units:** Widely used in arithmetic logic units (ALUs) and processors where fast addition is crucial.
- **Digital Signal Processing (DSP):** Used in DSP applications requiring rapid arithmetic operations.

12 Conclusion

The Carry Select Adder balances the trade-off between speed and complexity, providing a faster alternative to Ripple Carry Adders by leveraging parallel computation and selection logic. Its ability to quickly select the correct sum and carry-out makes it an essential component in high-speed arithmetic operations.